


BRAC University (Department of Computer Science and Engineering)
CSE 460 (VLSI Design) | Fall 2023

Assignment 1

1. Design the simplest sum-of-products circuit that implements the function $f(x_1, x_2, x_3) = \sum m(3, 4, 6, 7)$. **Using K-maps**
2. Design the simplest sum-of-products circuit that implements the function $f(x_1, x_2, x_3) = \sum m(1, 3, 4, 6, 7)$. **Using K-maps**
3. Design the simplest circuit that has three inputs, x_1 , x_2 , and x_3 , which produces an output value of 1 whenever exactly one or two of the input variables have the value 1; otherwise, the output has to be 0. [hint: you have to make the truth table first, then use K-map to simplify]
4. Repeat Problem 2 for the function $f(x_1, x_2, x_3) = m(1, 4, 7) + D(2, 5)$.
5. find the minimum sum-of-products expression for the function $f = x_1x_3 + x_1(x_2)' + (x_1)'x_2x_3 + (x_1)'(x_2)'(x_3)'$.
6. Consider the following circuit where an n-channel MOSFET in 180nm process is shown. The following parameters are given for the **M1**, **[7 Marks]**

$\mu_n C_{ox} = 100 \mu A/V^2$, $V_t = 0.5 V$, $V_{DD}=4V$, $V_D=1V$

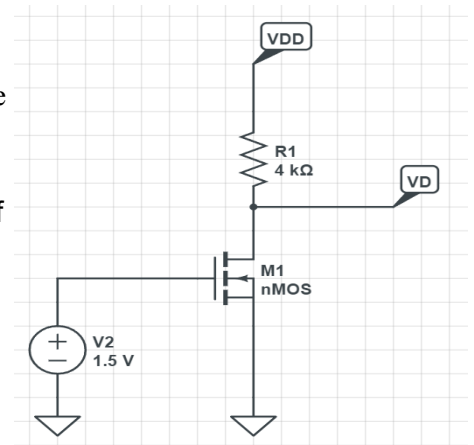- a. Calculate the current through the MOSFET and find the Necessary width W to attain that current.
- b. Again, assume that $W=1.8 \mu m$. Now find the value of **R1** that results in the given drain voltage V_D .



7. Explain the behavior/operating region of a MOS with following I-V characteristics at points A and B with necessary equations

